
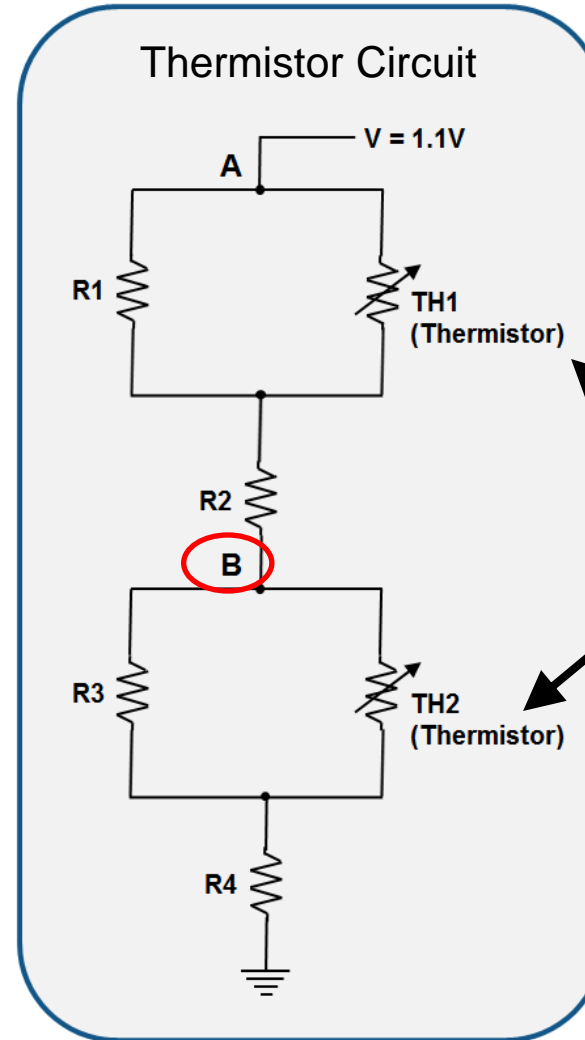


Demo: Optimal Component Selection Using Mixed-Integer Genetic Algorithm

Desired Voltage at Point B

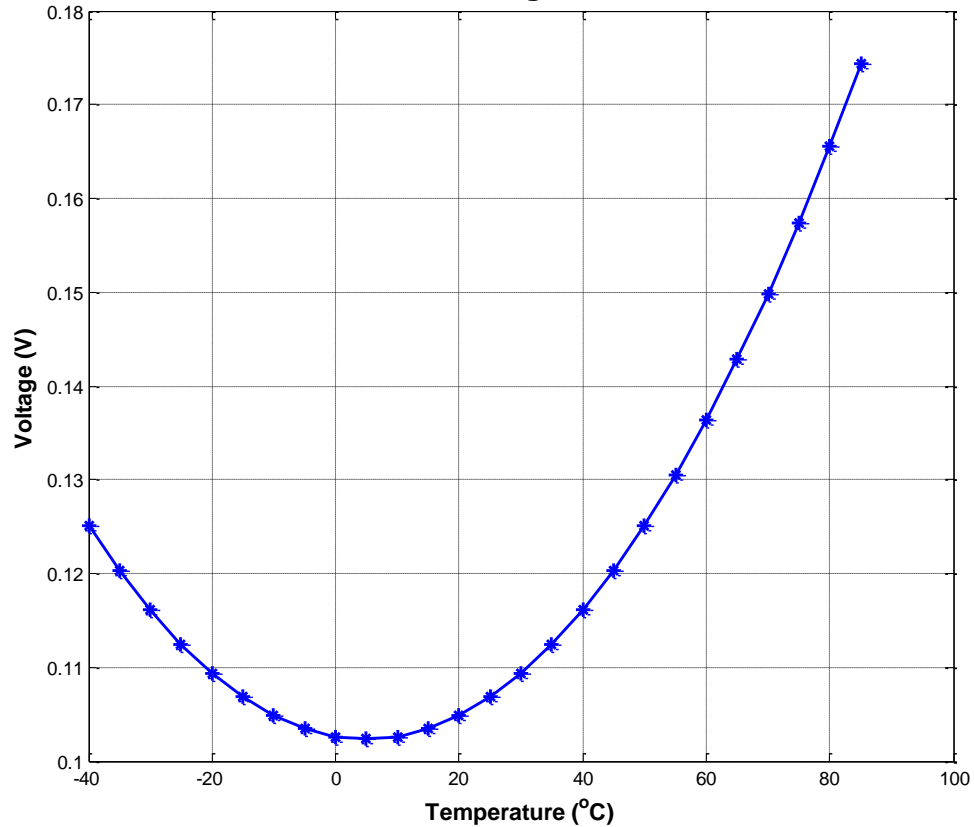

$$R_{TH} = \frac{R_N}{e^{\beta * \left(\frac{T - T_N}{T * T_N} \right)}}$$